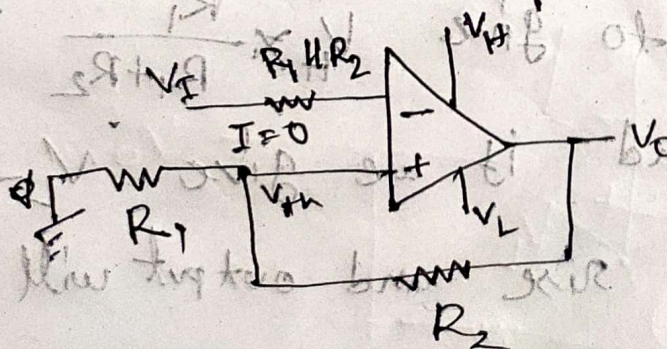



Inverting Schmitt trigger basic information:

The inverting Schmitt trigger circuit has an input signal applied to the negative terminal of a opamp, and output connected to the op-amp positive terminal and positive terminal connected to the ground and there is no current flow into the ~~input~~ op-amp but ~~the~~ output is connected to the ~~ground~~ and positive terminal so there is a current flow. The voltage is reference by ~~the~~ voltage V_H and V_L (Low). If $V_{in} > V_{th}$ then output is V_L and V_H (High). If $V_{in} < V_{th}$ then output is V_H .

The circuit:



Graph :

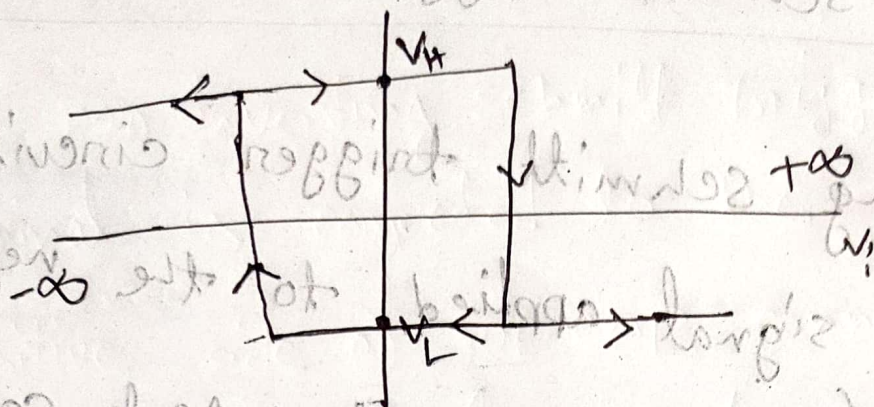

if the output voltage is lower than the

upper

if V_{in} is lower than the V_{th} then the output will be V_H (High). when we increase the

input voltage to then in a sudden point it reach V_{th} or bigger than V_{th} that time it will drop and output will be V_L (Low) for down


fall we need to give $V_H \times \frac{R_1}{R_1 + R_2}$ voltage.

on the other hand if we give $V_L \times \frac{R_1}{R_1 + R_2}$ voltage it will rise and output will be V_H .


Non-inverting schmitt Trigger basic information

In non-inverting schmitt Trigger the negative terminal is connected to the ground and positive side of op-amp connected to the input (V_I) terminal and also V_{in} connects to the V_O (output). and this amplifier reference by V_H (High) and V_L (Low). if input voltage is higher than the threshold voltage, V_O will be high. on the other hand input voltage is lower than threshold voltage, output will be low.

Circuit :

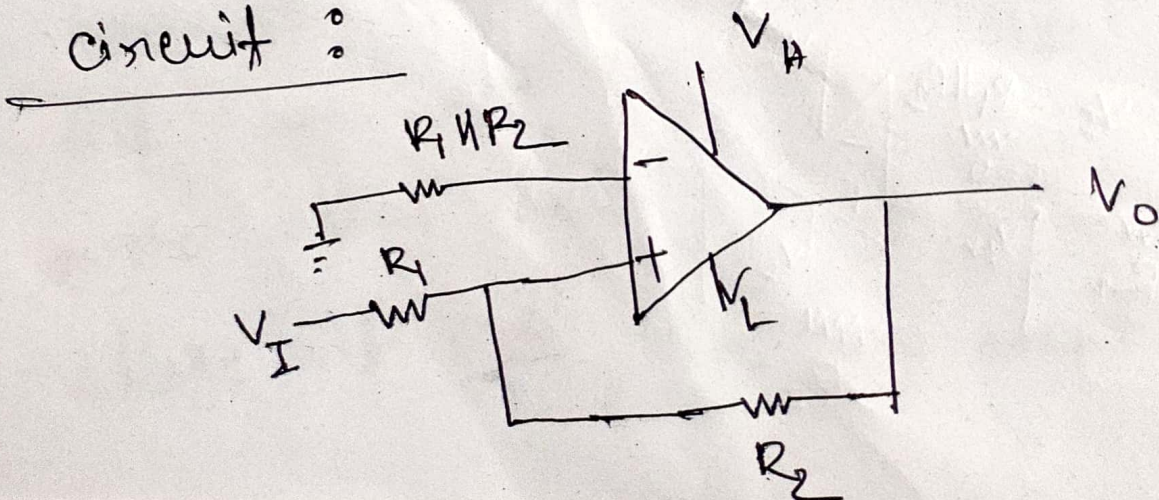

Graph:

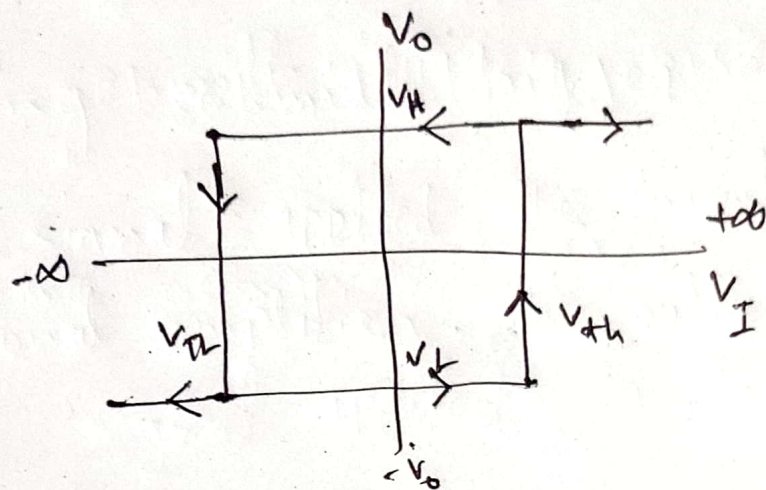

if the input voltage is extremely low then output (V_O) is low. when the $V_{th} = -V_L \frac{R_1}{R_2}$ reach to this voltage it will go to the V_H . on the other hand the input voltage is high then output (V_O) is ~~low~~ High.

and when $V_{th} \geq -V_H \frac{R_1}{R_2}$ reach this voltage it will drop and output will V_L .